

# C10 – Generic, generate

Yann DOUZE

## Port map

```
-- entité du composant COUNTER
entity COUNTER is
  port ( CLK, RST : in      Std_logic;
         UpDn    : in      Std_logic := '0';
         Q       : out     Std_logic_vector(2 downto 0));
end entity;

--Architecture STRUCT d'un composant BLOK instanciant COUNTER
architecture STRUCT of BLOK is
begin
  -- association par position
  G1 : entity work.COUNTER port map (Clk32MHz, RST, open, Count);
  -- association par nom
  G2 : entity work.COUNTER port map( RST => RST,
                                     CLK => Clk32MHz,
                                     Q(2) => Q1MHz,
                                     Q(1) => Q2MHz,
                                     Q(0) => Q4MHz);
end architecture;
```

Valeur par défaut

Non connecté

# 8位计数器 Compteur 8 bits

```
entity COUNTER8BIT is
    port ( CLK, RST : in      Std_logic;
           Q       : out      Std_logic_vector(7 downto 0));
end entity;
architecture RTL of COUNTER8BIT is
    signal CNT: unsigned(7 downto 0);
begin
    process (CLK,RST)
    begin
        if RST = '1' then
            CNT <= "00000000";
        elsif rising_edge(CLK) then
            CNT <= CNT + '1';
        end if;
    end process;
    Q <= std_logic_vector(CNT);
end architecture;
```

3

# 通用计数器 Compteur génériques

修改

```
entity COUNTER is
    generic (N: integer:=8);
    port ( CLK, RST : in      Std_logic;
           Q       : out      Std_logic_vector(N-1 downto 0));
end entity;
architecture RTL of COUNTER is
    signal CNT: unsigned(N-1 downto 0);
begin
    process (CLK,RST)
    begin
        if RST = '1' then
            CNT <= (others => '0');
        elsif rising_edge(CLK) then
            CNT <= CNT + '1';
        end if;
    end process;
    Q <= std_logic_vector(CNT);
end architecture;
```

修改这一处即可得到n位计数器。

4

## 例化通用组件

# Instanciation d'un composant générique

```
-- l'entité du composant COUNTER
entity COUNTER is
    generic(N : integer:=8);
    port (CLK, RST : in Std_logic;
          Q      : out Std_logic_vector(N-1 downto 0));
end entity;

-- Utilisé dans l'architecture STRUCT d'un composant BLOK
architecture STRUCT of BLOK is
    signal Count4: std_logic_vector(3 downto 0);
    signal Count6: std_logic_vector(5 downto 0);
begin
    -- association par position
    U1: entity work.COUNTER generic map (4)
    port map (CLK , RST, Count4);
    -- association par nom
    U2: entity work.COUNTER generic map (N => 6)
    port map (CLK => CLK, RST => RST, Q => Count6);
end architecture;
```

两个不同位  
的计数器

比一般例化出的行为。

5

## 通用延迟

# Les délais génériques

```
-- Entité du composant NAND2
entity NAND2 is
    generic(TPLH, TPHL: TIME := 0 NS);
    port (A, B: in Std_logic;
          F  : out Std_logic);
end entity;

-- Architecture STRUCT du composant BLOK
architecture STRUCT of BLOK is
    signal N1,N2,N3,N4,N5,N6,N7,N8,N9 : Std_logic;
begin
    G1: entity work.NAND2 generic map (1.9 NS, 2.8 NS)
    port map (N1, N2, N3);
    G2: entity work.NAND2 generic map (TPLH => 2 NS, TPHL => 3 NS)
    port map (A => N4, B => N5, F => N6);
    G3: entity work.NAND2 port map (A => N7, B => N8, F => N9);
end architecture;
```

默认模块

par défaut

6

# Instruction generate

通用指令 permet d'instancier plusieurs fois en composant  
可实例化组件.

```
architecture A1 of BLOK is
begin
  G1: for I in SOME_RANGE generate
    -- Instanciation de composant ou process
  end generate;

  G2: if CONDITION generate
    -- Instanciation de composant ou process
  end generate;

  --Exemple :
  G3: for I in 0 to 7 generate
    C1: entity work.COMP port map (D=>A(I), Q=>B(I));
  end generate;


end architecture;
```

常规结构

Structure optionnelle

可选结构

生成性语句

 

# Additionneur structurel générique

通用结构加法器

```
entity ADDN is
  generic (N: positive := 4);
  port (Cin : in std_logic;
        A,B : in std_logic_vector(N-1 downto 0);
        Cout : out std_logic;
        SUM: out std_logic_vector(N-1 downto 0));
end entity;

architecture STRUCT of ADDN is
  signal C : std_logic_vector(N downto 0);
begin
  C(0) <= Cin;

  L1: for I in A'range generate
    U1 : entity work.ADDC1 port map (
      Cin => C(I), A => A(I), B => B(I),
      SUM => SUM(I), Cout => C(I+1));
  end generate;

  Cout <= C(N);
end architecture;
```

